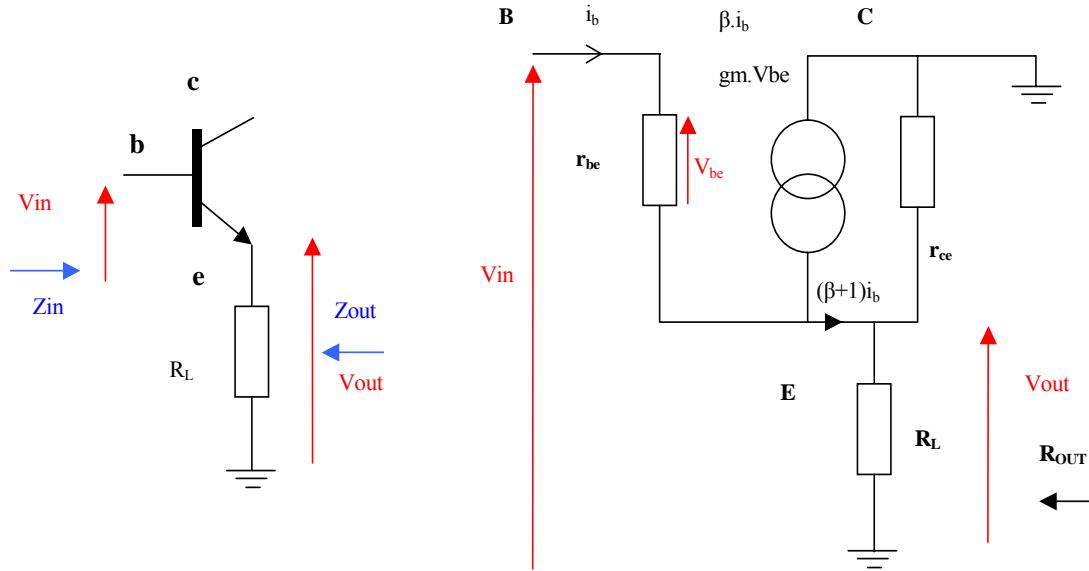


Common-Collector/Drain Circuits

Common-Collector Drain BJT Circuit

Figure 1 below shows the simplified 'Pi' model of a common-collector BJT.



$$R_L' = \frac{r_{ce} \cdot R_L}{r_{ce} + R_L} \quad \frac{1}{R_L'} = \frac{1}{r_{ce}} + \frac{1}{R_L} = g_o + g_L$$

$$R_{IN} = \frac{V_{IN}}{I_{IN}} = \frac{V_{be} + V_{RL}}{I_b} = \frac{r_{be} \cdot I_b + R_L'(\beta + 1) \cdot I_b}{I_b} = r_{be} + R_L'(\beta + 1) \approx \beta \cdot R_L'$$

$$R_{OUT} = \frac{V_{OUT}}{I_{OUT}} = \frac{(\beta + 1) \cdot i_b \cdot R_L'}{(\beta + 1) \cdot i_b} = R_L' = \frac{r_{ce} \cdot R_L}{r_{ce} + R_L} \quad \text{if } R_L \ll r_{ce} \text{ then } R_{OUT} \approx r_{ce}$$

$$A_V = \frac{V_{OUT}}{V_{IN}} = \frac{R_L'(\beta + 1) \cdot I_b}{r_{be} \cdot I_b + R_L'(\beta + 1) \cdot I_b} = \frac{R_L'(\beta + 1)}{r_{be} + R_L'(\beta + 1)} \quad \text{divide top \& bottom by } (\beta + 1)$$


$$A_V = \frac{R_L'}{r_{be} + R_L'} \quad r_{be} = \frac{\beta}{gm} \quad \therefore A_V = \frac{R_L'}{\frac{1}{gm} \cdot \frac{\beta}{(\beta + 1)} + R_L'} \quad \text{from above } \frac{1}{R_L'} = g_o + g_L$$

$$A_V = \frac{\frac{1}{g_o + g_L}}{\frac{1}{gm} \cdot \frac{\beta}{(\beta + 1)} + \frac{1}{g_o + g_L}} \quad \text{Multiply top \& bottom by } g_o + g_L = \frac{1}{\frac{1}{gm} \cdot \frac{\beta}{(\beta + 1)} + 1}$$

Let $\alpha = \frac{\beta}{\beta + 1}$ and let $\delta = \frac{g_o + g_L}{g_m}$ $A_v = \frac{1}{1 + \alpha \cdot \delta}$

$A_i = \frac{I_{OUT}}{I_{IN}} = \frac{(\beta + 1)i_b}{i_b} = (\beta + 1) \approx \beta$

Common-Drain MOS FET Circuit

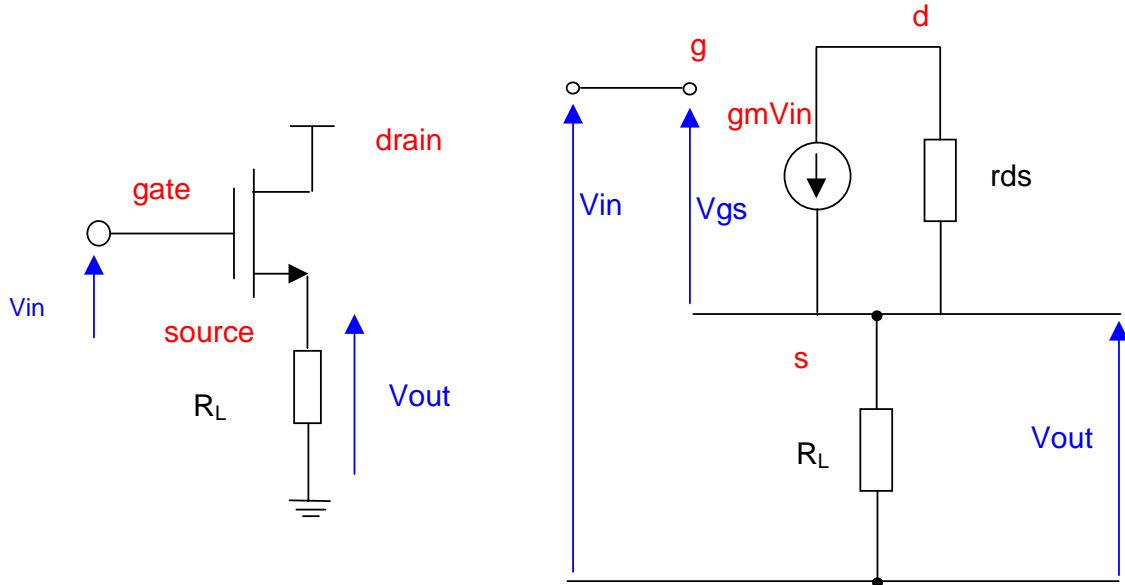

Voltage Gain Av

$A_v = \frac{V_o}{V_{IN}} = \frac{V_o}{V_{gs} + V_o}$

$V_o = gmV_{gs}(r_{ds} // R_L)$ $A_v = \frac{gmV_{gs}(r_{ds} // R_L)}{V_{gs} + gmV_{gs}(r_{ds} // R_L)}$ divide top & bottom by V_{gs}

$A_v = \frac{gm(r_{ds} // R_L)}{1 + gm(r_{ds} // R_L)}$ $A_v = gm(r_{ds} // R_L)$ Therefore, $A_v = \frac{A}{1 + A} \approx 1$

Input Resistance

$R_{IN} = \infty$

Output Resistance

$R_{OUT} = \frac{V_o}{I_o} = \frac{1}{gm}$

Current Gain Ai

$A_i = \infty$